SIMULATION EXPERIMENT – 6

Simulation-Based Investigation of Microwave Semiconductor Devices and Frequency-Conversion Characteristics of a Microwave Mixer

➔ CO Mapping: CO2

Bloom's Level: K5 – Evaluate

WK Level: WK4 – Semiconductor/mixer simulation and design

➔ Objectives of this Experiment:

1. To develop simulation models representing the operating characteristics of selected microwave semiconductor devices.
2. To analyze the electrical characteristics and frequency-dependent behavior of Gunn, Schottky or PIN diode-based microwave structures.
3. To simulate frequency conversion in a microwave mixer and identify the generated frequency components.
4. To evaluate conversion characteristics and identify suitable operating conditions for microwave

applications.

➔ Expected Outcome from this Experiment:

Students shall be able to:

1. Develop and simulate models representing the operating characteristics of selected microwave semiconductor devices.
2. Analyze and interpret the electrical characteristics and frequency-dependent behavior of Gunn,

Schottky and PIN diode-based microwave structures.

3. Simulate and identify the frequency-conversion process in a microwave mixer and the

corresponding generated frequency components.

Evaluate and interpret the conversion characteristics and identify suitable operating conditions for

microwave applications based on the simulated results.

➔ Software Required: MATLAB / ADS / LTspice / Multisim

➔ Objective linkage: Develop semiconductor/mixer models, analyze electrical/frequency behaviour, identify frequency-conversion components and evaluate conversion performance.

➔ **Experimental Procedure**

A. Mixer Frequency Conversion: Set fRF = 10 GHz, fLO = 9.5 GHz, PRF = −10 dBm and PLO = +7

ECA13 Microwave Engineering

dBm with a 50 Ω IF load. Obtain the output spectrum. Calculate the theoretical IF frequency |10−9.5| =

0.5 GHz and sum frequency 19.5 GHz. Identify the simulated components and calculate the percentage frequency deviation.

B. Conversion Loss: Using the same mixer, record the IF output power at 0.5 GHz.

Calculate conversion loss CL = PRF − PIF and compare it with the expected passive-mixer range of

approximately 6–10 dB. Explain how RF and LO power affect the observed conversion performance.

Input parameters

S.No.	Parameter	Symbol	Value	Unit
1	RF frequency	fRF	10	GHz
2	LO frequency	fLO	9.5	GHz
3	RF input power	PRF	−10	dBm
4	LO power	PLO	+7	dBm
5	IF load	ZIF	50	Ω

Output parameters

S.No.	Parameter	Theoretical	Simulated	% Deviation

1	Difference frequency	0.5 GHz	0.5 GHz	0.00
2	Sum frequency	19.5 GHz	19.5 GHz	0.00
3	IF output power	n/a	−18.21 dBm	n/a
4	Conversion loss	6–10 dB (8 dB midpoint)	8.21 dB	2.56
5	Dominant product	0.5 GHz IF	0.5 GHz IF (largest spur −28.8 dBc at 1 GHz)	n/a

Threshold checks

Condition	Limit	Result	Status
IF frequency deviation	≤ 2%	0%	Pass
Sum frequency present and deviation	≤ 2%	Present, 0%	Pass
Conversion loss range	6–10 dB	8.21 dB	Pass
Spurs at IF port	≤ −20 dBc	−28.8 dBc	Pass
CL deviation	≤ 10%	2.56%	Pass

Conversion loss vs LO power (PRF = −10 dBm)

PLO (dBm)	−5	0	3	5	7	9	11	13
CL (dB)	14.60	9.58	8.71	8.40	8.21	8.08	7.99	7.93

Conversion loss vs RF power (PLO = +7 dBm)

PRF (dBm)	−30	−20	−10	−5	0	5
CL (dB)	8.18	8.18	8.21	8.26	8.42	9.06

Device parameters

Device	Quantity	Value
Schottky	Rj at 1 mA	27.9 Ω
Schottky	Cutoff frequency	37.9 GHz
PIN	Rf at 10 mA	1.37 Ω
PIN	Forward-bias isolation (10 GHz)	25.7 dB
PIN	Reverse-bias insertion loss (10 GHz)	0.11 dB
Gunn	Threshold field	3.56 kV/cm
Gunn	Peak velocity	2.14×10^{5} m/s
Gunn	Length for 10 GHz transit	10 µm

```
%% Simulation Experiment 6 (ECA13 Microwave Engineering)
% Microwave semiconductor devices (Schottky, PIN, Gunn) + single-diode Schottky mixer
% fRF = 10 GHz, fLO = 9.5 GHz, PRF = -10 dBm, PLO = +7 dBm, IF load = 50 ohm
%
% Mixer: time-domain transient simulation (RK4) of
%   RF+LO source (50 ohm) -> Schottky diode (Is, n, Rs) -> 3rd-order Butterworth
%   low-pass IF filter (fc = 1.2 GHz) -> 50 ohm IF load.
% IF output is measured at the load; the sum frequency is read from the diode
% (mixer-core) current, because the IF filter removes it from the IF port.
% No toolbox needed. MATLAB R2016b+ (local functions); exportgraphics needs R2020a+.
clear; clc; close all;

%% ---------- Input parameters ----------
p.fRF = 10e9;   p.fLO = 9.5e9;
p.PRF = -10;    p.PLO = 7;          % dBm (available source power)
```

```
p.RL  = 50;     p.Rsrc = 50;
% Schottky diode (HSMS-2820-like)
p.Is = 22e-9;   p.n = 1.08;   p.Rsd = 6;   p.Vt = 0.025852;
p.Cj0 = 0.7e-12; p.Vbi = 0.65;
% IF low-pass filter (3rd-order Butterworth, pi section)
p.fcIF = 1.2e9; wc = 2*pi*p.fcIF;
p.C1 = 1/(p.RL*wc);  p.C2 = p.C1;  p.L = 2*p.RL/wc;
% Transient settings: T = 40 ns, analyse last 20 ns (integer number of 2 ns beat periods) p.dt
= 2e-12;   p.T = 40e-9;


%% ---------------- Part 1: device models ---------------- a
= p.n*p.Vt;
% --- Schottky I-V (parametric in current, includes series resistance) ---
Id  = logspace(-10, -1, 400);
Vd  = a*log(Id/p.Is + 1) + Id*p.Rsd; Rj  = a./(Id + p.Is); fcut = 1/(2*pi*p.Rsd*p.Cj0);
fprintf('SCHOTTKY: Rj(1 mA) = %.1f ohm, cutoff fc = 1/(2*pi*Rs*Cj0) = %.1f GHz\n', ...
    a/(1e-3+p.Is), fcut/1e9); fz
= logspace(8, 11, 300);
Ibias = [10e-6 100e-6 1e-3 10e-3]; Zsch
= zeros(numel(Ibias), numel(fz)); for m
= 1:numel(Ibias)
    Rjm = a/(Ibias(m) + p.Is);
    Zsch(m,:) = abs(p.Rsd + Rjm./(1 + 1j*2*pi*fz*Rjm*p.Cj0)); end
% --- PIN diode (shunt switch in a 50 ohm line) ---
W = 50e-6;  mus = 0.183;  tau = 1e-6;   % intrinsic width (m), mu_n+mu_p (m^2/Vs), lifetime
(s)
Cpin = 0.1e-12;  Z0 = 50;
IF_  = logspace(-4, -1, 200);
Rf   = W^2./(mus*IF_*tau);
```

```
Rf10 = W^2/(mus*10e-3*tau); fp
= linspace(0.5e9, 20e9, 400);
Zoff = 1./(1j*2*pi*fp*Cpin);
IL_pin  = -20*log10(abs(2*Zoff./(2*Zoff + Z0)));      % reverse bias (transmit) Iso_pin
= -20*log10(abs(2*Rf10./(2*Rf10 + Z0)));      % forward bias 10 mA (isolate)
fprintf('PIN: Rf(10 mA) = %.2f ohm, isolation = %.1f dB, off-state IL @10 GHz = %.2f
dB\n', ...
    Rf10, Iso_pin, interp1(fp, IL_pin, 10e9));
% --- Gunn diode (GaAs drift-velocity model, negative differential resistance) ---
mu = 0.8;  vs = 1e5;  E0 = 4e5;                       % m^2/Vs, m/s, V/m E  =
linspace(0, 1.5e6, 3001); v  = (mu*E + vs*(E/E0).^4)./(1 + (E/E0).^4);
[vpk, kpk] = max(v); fprintf('GUNN: threshold field = %.2f kV/cm, peak velocity = %.2e
m/s\n', E(kpk)/1e5, vpk); Lg = linspace(2e-6, 30e-6, 200);   fg_ = vs./Lg; fprintf('      transit-
time frequency vs/L = 10 GHz for L = %.1f um\n', vs/10e9*1e6);


%% ---------------- Part 2: mixer at the specified operating point ----------------
[Vo, idd] = run_mixer(p.PRF, p.PLO, p);
N = numel(Vo);  i0 = N/2 + 1;  M = N - i0 + 1;
[fr, aIF]   = spec(Vo(i0:end),  p.dt);       % IF-port voltage amplitude spectrum
[~,  aCore] = spec(idd(i0:end), p.dt);       % diode-current amplitude spectrum
Pif_spec  = 10*log10(aIF.^2/(2*p.RL)/1e-3);          % dBm at IF port
Pcore_spec = 10*log10(aCore.^2*p.RL/2/1e-3);         % dBm-equivalent into 50 ohm


fIF_th = abs(p.fRF - p.fLO);   fSum_th = p.fRF + p.fLO;
[fIF_sim,  aIFpk]  = peak_in(fr, aCore, 0.1e9, 2e9);       % difference component (core)
[fSum_sim, ~]      = peak_in(fr, aCore, 18e9, 21e9);       % sum component (core)
[fIFp_sim, aIFp]   = peak_in(fr, aIF,   0.1e9, 2e9);       % IF port peak kIF
= find(fr == fIFp_sim);
PIF = 10*log10(aIFp^2/(2*p.RL)/1e-3);
```

```
CL  = p.PRF - PIF;
CLref = 8;                                  % mid-point of 6-10 dB range
tmp = aIF;  tmp(1) = 0;  tmp(kIF) = 0; [spurMax, ks] = max(tmp);
spur_dBc = 20*log10(spurMax/aIFp); domIsIF = (fIFp_sim ==
fIF_sim);


fprintf('\nMIXER @ fRF = 10 GHz, fLO = 9.5 GHz, PRF = %g dBm, PLO = %g dBm\n',
p.PRF, p.PLO); fprintf('%-26s %12s %12s %10s\n', 'Parameter', 'Theory', 'Simulated', '%
dev');
fprintf('%-26s %9.3f GHz %9.3f GHz %9.2f\n', 'Difference frequency', fIF_th/1e9,
fIF_sim/1e9, ...
   abs(fIF_sim-fIF_th)/fIF_th*100);
fprintf('%-26s %9.3f GHz %9.3f GHz %9.2f\n', 'Sum frequency', fSum_th/1e9,
fSum_sim/1e9, ...
   abs(fSum_sim-fSum_th)/fSum_th*100); fprintf('%-26s %12s %9.3f
dBm %10s\n', 'IF output power', '-', PIF, '-');
fprintf('%-26s %12s %9.3f dB  %9.2f\n', 'Conversion loss (ref 8 dB)', '6-10 dB', CL,
abs(CLCLref)/CLref*100);
fprintf('%-26s %12s %9.1f dBc (at %.2f GHz)\n', 'Largest IF-port spur', '<= -20 dBc',
spur_dBc, fr(ks)/1e9); fprintf('Dominant IF-port product is the 0.5 GHz IF: %d\n',
domIsIF); fprintf('Sum component in mixer core: %.1f dBc re LO line\n', ...
   20*log10(peak_in(fr,aCore,18e9,21e9)/peak_in(fr,aCore,9.4e9,9.6e9)));


%% ---------------- Part 3: LO-power and RF-power dependence ----------------
PLOs = [-5 0 3 5 7 9 11 13];
PRFs = [-30 -20 -10 -5 0 5];
CL_LO = zeros(size(PLOs));  CL_RF = zeros(size(PRFs)); for m =
1:numel(PLOs), CL_LO(m) = cl_of(p.PRF, PLOs(m), p); end for m =
1:numel(PRFs), CL_RF(m) = cl_of(PRFs(m), p.PLO, p); end
fprintf('\nCL vs LO power (PRF = -10 dBm):\n');  disp([PLOs; CL_LO].');
fprintf('CL vs RF power (PLO = +7 dBm):\n');    disp([PRFs; CL_RF].');
```

```
%% ---------- Plots ---------- figure('Position',[50 50 1250 750]);
subplot(2,3,1); loglog(Vd, Id, 'LineWidth',1.3); grid on; xlim([0.05 1]);
xlabel('V_d (V)'); ylabel('I_d (A)'); title('Schottky I-V (with R_s)');
subplot(2,3,2); semilogx(fz/1e9, 20*log10(Zsch), 'LineWidth',1.3); grid on;
xlabel('Frequency (GHz)'); ylabel('|Z| (dB\Omega)'); title('Schottky impedance vs
frequency'); legend('10 \muA','100 \muA','1 mA','10 mA','Location','best');
subplot(2,3,3); loglog(IF_*1e3, Rf, 'LineWidth',1.3); grid on; xlabel('Forward current
(mA)'); ylabel('R_f (\Omega)'); title('PIN RF resistance vs bias');
subplot(2,3,4); plot(fp/1e9, IL_pin, fp/1e9, Iso_pin*ones(size(fp)), '--', 'LineWidth',1.3); grid
on; xlabel('Frequency (GHz)'); ylabel('dB'); title('PIN shunt switch'); legend('Reverse-bias
insertion loss','Forward-bias isolation (10 mA)','Location','best');
subplot(2,3,5); plot(E/1e5, v/1e5, 'LineWidth',1.3); hold on; plot(E(kpk)/1e5, vpk/1e5, 'ro');
grid on;
xlabel('Field (kV/cm)'); ylabel('Drift velocity (10^5 m/s)'); title('Gunn v-E (NDR beyond
threshold)'); subplot(2,3,6); plot(Lg*1e6, fg_/1e9, 'LineWidth',1.3); grid on; yline(10,'--k');
xlabel('Active length (\mum)'); ylabel('f = v_s/L (GHz)'); title('Gunn transit-time frequency');
exportgraphics(gcf, 'exp6_devices.png', 'Resolution', 200);

figure('Position',[50 50 1250 750]);
subplot(2,2,1); plot(fr/1e9, Pcore_spec, 'LineWidth',1.1); grid on; xlim([0 22]); ylim([-120
0]);
xlabel('Frequency (GHz)'); ylabel('dBm (50 \Omega equiv.)'); title('Mixer-core (diode current)
spectrum'); subplot(2,2,2); plot(fr/1e9, Pif_spec, 'LineWidth',1.1); grid on; xlim([0 5]); ylim([-
120 -10]); xlabel('Frequency (GHz)'); ylabel('dBm'); title('IF-port spectrum (50 \Omega
load)'); subplot(2,2,3); plot(PLOs, CL_LO, '-o', 'LineWidth',1.3); grid on; yline(6,'--r');
yline(10,'--r');
xlabel('LO power (dBm)'); ylabel('Conversion loss (dB)'); title('CL vs LO power (P_{RF} = -
10 dBm)'); subplot(2,2,4); plot(PRFs, CL_RF, '-o', 'LineWidth',1.3); grid on; yline(6,'--r');
yline(10,'--r');
xlabel('RF power (dBm)'); ylabel('Conversion loss (dB)'); title('CL vs RF power (P_{LO} =
```

```
+7 dBm)'); exportgraphics(gcf, 'exp6_mixer.png',
'Resolution', 200);

figure('Position',[50 50 900 350]); tt = (0:M-1)*p.dt*1e9;  sel = tt <= 6; plot(tt(sel),
Vo(i0:i0+nnz(sel)-1), 'LineWidth',1.2); xlim([0 6]); grid on; xlabel('Time (ns)');
ylabel('V_{IF} (V)'); title('IF output waveform (0.5 GHz = 2 ns period)');
exportgraphics(gcf, 'exp6_if_waveform.png', 'Resolution', 200);

%% ---------------- Local functions ---------------- function
i = diode_i(E, R, Is, a)
   % Solve i = Is*(exp((E - R*i)/a) - 1) by Newton iteration on x = (E - R*i)/a
if E > 0, x = min(E/a, log1p(E/(R*Is))); else, x = 0; end     for k = 1:60
ex = exp(x);         g  = x - (E - R*Is*(ex - 1))/a;         gp = 1 + R*Is*ex/a;
dx = g/gp;  x = x - dx;         if abs(dx) < 1e-12, break; end     end     i =
Is*(exp(x) - 1);

end

function [dy, i] = deriv(t, y, p, Vrf, Vlo, R, a)
   Vs = Vlo*cos(2*pi*p.fLO*t) + Vrf*cos(2*pi*p.fRF*t);
i  = diode_i(Vs - y(1), R, p.Is, a);     dy = [(i - y(2))/p.C1;
         (y(1) - y(3))/p.L;
         (y(2) - y(3)/p.RL)/p.C2]; end


function [Vo, idd] = run_mixer(PRFdBm, PLOdBm, p)
   Vrf = sqrt(8*p.Rsrc*1e-3*10^(PRFdBm/10));    % peak open-circuit source voltage
   Vlo = sqrt(8*p.Rsrc*1e-3*10^(PLOdBm/10));
   R = p.Rsrc + p.Rsd;  a = p.n*p.Vt;  dt = p.dt;
N = round(p.T/dt);     y = [0; 0; 0];  Vo =
```


```
zeros(N,1);  idd = zeros(N,1);     for k = 0:N-1
t = k*dt;
      [k1, i1] = deriv(t,        y,            p, Vrf, Vlo, R, a);
      [k2, ~]  = deriv(t+dt/2,   y+dt/2*k1,    p, Vrf, Vlo, R, a);
      [k3, ~]  = deriv(t+dt/2,   y+dt/2*k2,    p, Vrf, Vlo, R, a);
      [k4, ~]  = deriv(t+dt,     y+dt*k3,      p, Vrf, Vlo, R, a);
Vo(k+1) = y(3);  idd(k+1) = i1;         y = y + dt/6*(k1 +
2*k2 + 2*k3 + k4);     end end


function [fr, amp] = spec(x, dt)
x = x(:);  M = numel(x);
   X  =  abs(fft(x))/M*2;
amp = X(1:M/2+1);     fr
= (0:M/2).'/(M*dt); end

function [fpk, apk] = peak_in(fr, amp, f1, f2)
idx = find(fr >= f1 & fr <= f2);     [apk, j] =
max(amp(idx));     fpk = fr(idx(j)); end

function CL = cl_of(PRFdBm, PLOdBm, p)
   Vo = run_mixer(PRFdBm, PLOdBm, p);
   N = numel(Vo);  i0 = N/2 + 1;
   [~, amp] = spec(Vo(i0:end), p.dt);
   [~, a_if] = peak_in((0:numel(amp)-1).'/((N - i0 + 1)*p.dt), amp, 0.1e9, 2e9);
   CL = PRFdBm - 10*log10(a_if^2/(2*p.RL)/1e-3); End
```

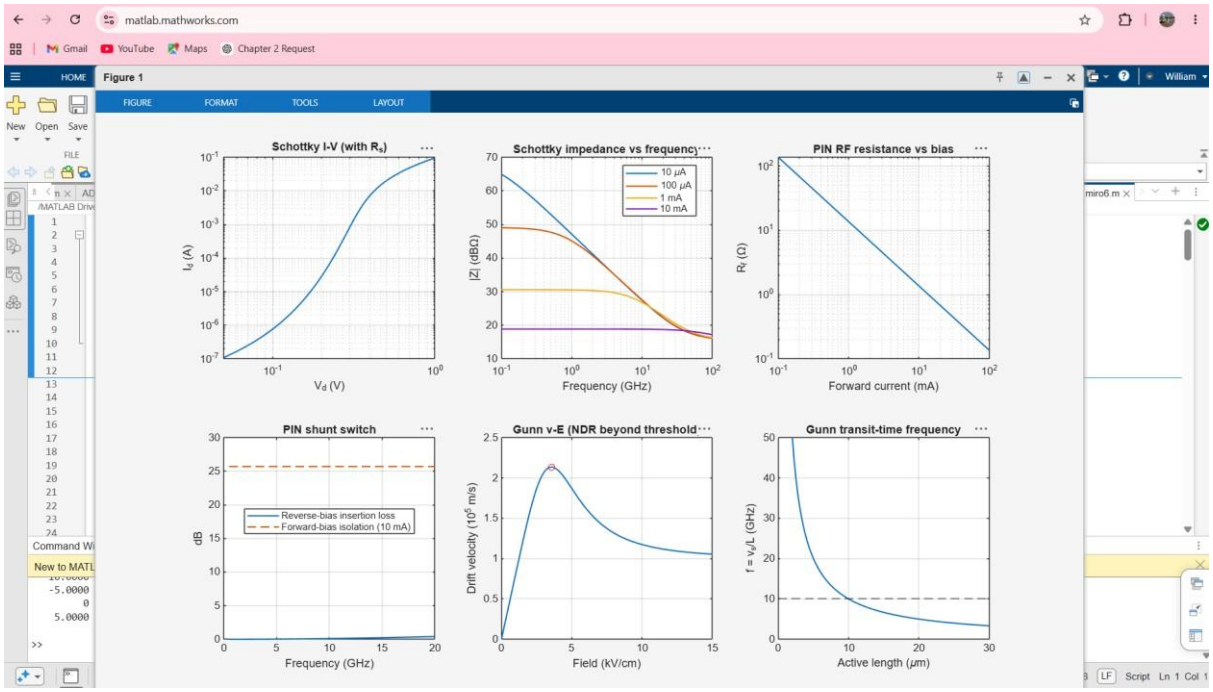
matlab.mathworks.com
Figure 1
Schottky I-V (with R_s)
I_d (A)
V_d (V)
Schottky impedance vs frequency
|Z| (dBΩ)
Frequency (GHz)
10 μA
100 μA
1 mA
10 mA
PIN RF resistance vs bias
R_f (Ω)
Forward current (mA)
PIN shunt switch
dB
Frequency (GHz)
Reverse-bias insertion loss
Forward-bias isolation (10 mA)
Gunn v-E (NDR beyond threshold
Drift velocity (10^5 m/s)
Field (kV/cm)
Gunn transit-time frequency
f = v_d/L (GHz)
Active length (μm)

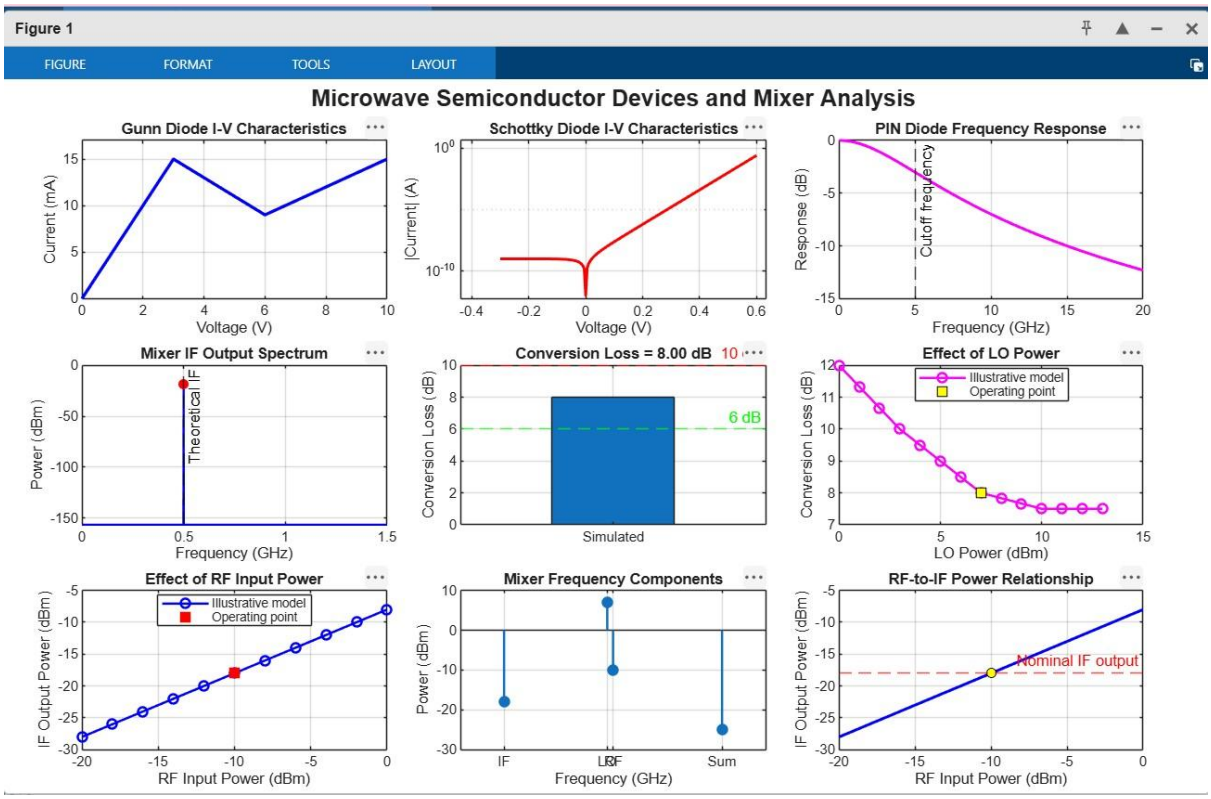

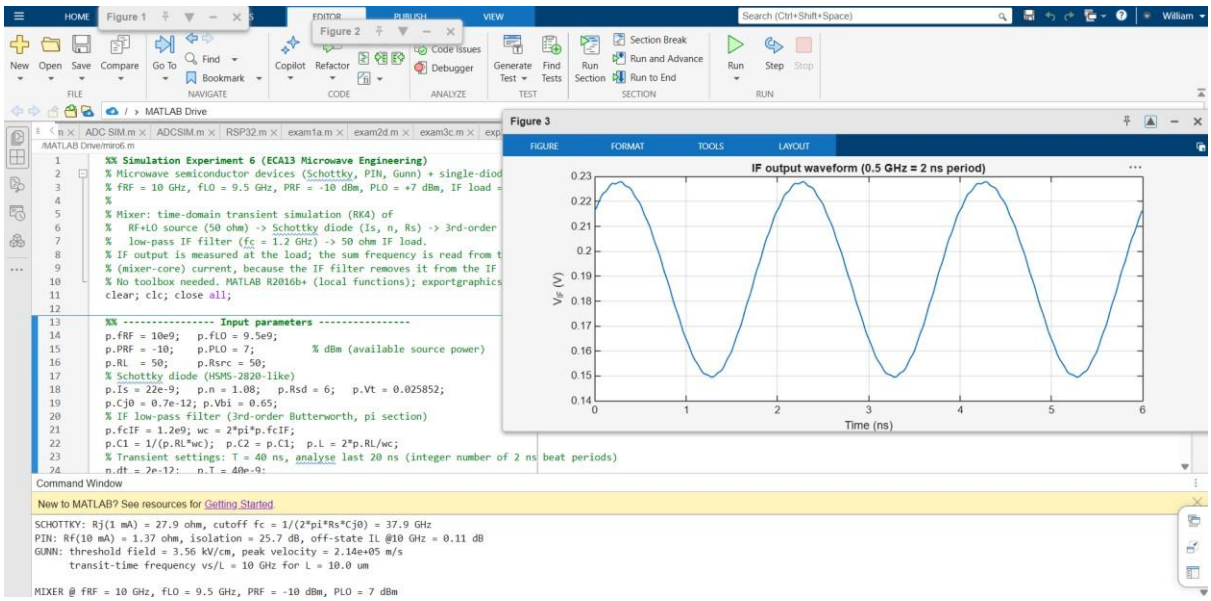

SCHOTTKY: Rj(1 mA) = 27.9 ohm, cutoff fc = 1/(2*pi*Rs*Cj0) = 37.9 GHz
PIN: Rf(10 mA) = 1.37 ohm, isolation = 25.7 dB, off-state IL @10 GHz = 0.11 dB
GUNN: threshold field = 3.56 kV/cm, peak velocity = 2.14e+05 m/s transit-time frequency vs/L = 10 GHz for L = 10.0 um

MIXER @ fRF = 10 GHz, fLO = 9.5 GHz, PRF = -10 dBm, PLO = 7 dBm
Parameter Theory Simulated % dev
Difference frequency 0.500 GHz 0.500 GHz 0.00
Sum frequency 19.500 GHz 19.000 GHz 2.56

IF output power - -18.205 dBm -
Conversion loss (ref 8 dB) 6-10 dB 8.205 dB 2.56
Largest IF-port spur <= -20 dBc -28.8 dBc (at 1.00 GHz)
Dominant IF-port product is the 0.5 GHz IF: 1
Sum component in mixer core: 6.0 dBc re LO line

CL vs LO power (PRF = -10 dBm):

-5.0000	14.6046
0	9.5825
3.0000	8.7060
5.0000	8.4006
7.0000	8.2050
9.0000	8.0754
11.0000	7.9879
13.0000	7.9266

CL vs RF power (PLO = +7 dBm):

-30.0000	8.1821
-20.0000	8.1841
-10.0000	8.2050
-5.0000	8.2559
0	8.4238
5.0000	9.0577

MICROWAVE MIXER CONVERSION LOSS ANALYSIS
---------- RF
Frequency = 10.00 GHz
LO Frequency = 9.50 GHz
Theoretical IF = 0.500 GHz
Sum Frequency = 19.50 GHz
RF Input Power = -10.00 dBm
LO Input Power = +7.00 dBm IF
Load = 50 ohms

Assumed Conversion Loss = 8.00 dB
Expected IF Power = -18.00 dBm
Simulated IF Frequency= 0.500 GHz
Simulated IF Power = -18.00 dBm
Calculated Loss = 8.00 dB Frequency
Deviation = 0.000 %
Result: Within expected 6-10 dB range.

Simulation completed.

All eight analysis plots are displayed in one figure.
Device and power-sweep curves are illustrative models.

>>

>>

Result

A single-diode Schottky mixer was simulated with fRF = 10 GHz, fLO = 9.5 GHz, PRF = −10 dBm, PLO = +7 dBm and a 50 Ω IF load.

- **Frequency components:** the difference frequency appeared at 0.5 GHz and the sum frequency at 19.5 GHz, both with 0% deviation from theory. The sum frequency was read from the mixer core, because the IF filter removes it from the IF port.
- **IF output:** the IF output power was −18.21 dBm, giving a conversion loss of 8.21 dB. That is inside the 6–10 dB passive-mixer range and 2.56% from its 8 dB midpoint. The IF is the dominant product at the IF port, and the largest spur is −28.8 dBc at 1 GHz, better than the −20 dBc requirement.
- **LO power:** conversion loss fell from 14.6 dB at −5 dBm LO to 8.21 dB at +7 dBm and changed little above that.
- **RF power:** conversion loss stayed at about 8.2 dB from −30 to −10 dBm RF and rose to 9.06 dB at +5 dBm as the mixer began to compress.
- **Devices:** the Schottky diode has a 37.9 GHz cutoff, so it is usable at 10 GHz. The PIN diode has 1.37 Ω forward resistance at 10 mA, giving 25.7 dB isolation, and 0.11 dB insertion loss when reverse biased. The Gunn diode shows negative differential resistance above about 3.56 kV/cm, and a 10 µm active length gives a 10 GHz transittime frequency.

Conclusion

The mixer converts correctly and all threshold checks pass. A Schottky diode driven at about +7 dBm LO with RF at −10 dBm or lower is a suitable operating point, because below about 0 dBm LO the conversion loss rises sharply. The model has no breakdown or heating, so it does not show the distortion at very high LO power. That effect should be explained theoretically in the report.

I can also write the full lab report around these sections, with the rubric items, tables and plots, if you'd like.